



GAYATRI VIDYA PARISHAD COLLEGE OF ENGINEERING (Autonomous)

Approved by AICTE & Affiliated to Andhra University, Visakhapatnam from 2022-23

(Affiliated to JNTU R. Kakinada upto 2021-22)

Re-accredited by NAAC twice with 'A' Grade with a CGPA of 3.47/4.00

Madhurawada, Visakhapatnam - 530048

B. Tech. I Semester


Branch: CSE

Course Title	Basic Electrical & Electronics Engineering	Course Code	20EE11D3
Date	11-01-2023	Academic Year	2022-23
Time	90 min	Max. Marks	30

	1(a)	1(b)	2(a)	2(b)	3(a)	3(b)	4(a)	4(b)	5(a)	5(b)	6(a)	6(b)	Total Marks
CO	1	1	1	1	2	2	2	2	1	2	1	2	
Marks													

Answer All the Questions

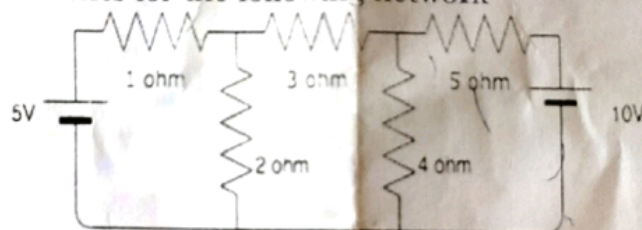- 1(a) State and explain Kirchhoffs laws ✓
(b) Obtain the mesh currents for the following network ✓




3x10=30M

5M

5M


(OR)

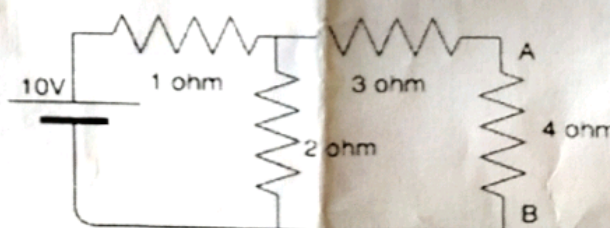- 2(a) Obtain the thevinins equivalent between the terminals A and B



5M

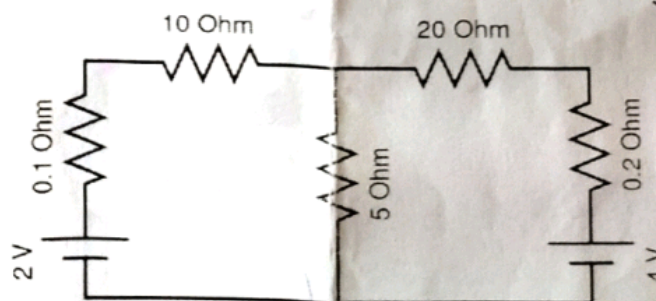- (b) Find the current in 5 ohm resistor using superposition theorem ✓



5M

- 3(a) Derive the emf equation of DC generator
(b) Draw and explain the performance characteristics of DC Generator (OR)

5M

5M

- 4(a) Derive the torque equation of DC Motor
(b) Explain the performance characteristics of DC Motor

5M

5M

Roll No.

3 2 2 1 0 3 3 1 0 0 2 2



GAYATRI VIDYA PARISHAD COLLEGE OF ENGINEERING (Autonomous)


Approved by AICTE & Affiliated to Andhra University, Visakhapatnam from 2022-23

(Affiliated to JNTUK, Kakinada upto 2021-22)

Re-accredited by NAAC twice with 'A' Grade with a CGPA of 3.47/4.00

Madhurawada, Visakhapatnam - 530048

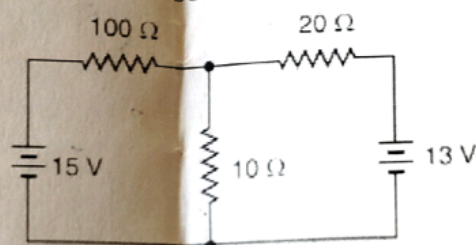
- 5(a) Apply source transformation to the entire network and obtain (voltage source in series with resistance or current source in parallel to resistance) 5M



- (b) An 8-pole d.c. generator has 500 armature conductors, and a useful flux of 0.05 Wb per pole. What will be the e.m.f. generated if it is lap-connected and runs at 1200 rpm? What must be the speed at which it is to be driven produce the same e.m.f. if it is wave-wound? 5M

(OR)

- 6(a) Obtain the node voltages

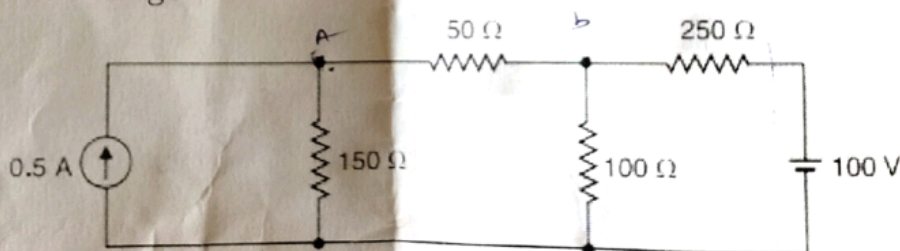

- (b) In a brake test the effective load on the branch pulley was 38.1 kg, the effective diameter of the pulley 63.5 cm and speed 12 r.p.s. The motor took 49 A at 220 V. Calculate the output power and the efficiency at this load. 5M

$$0.591 \times 2 \times 51.52$$